


# ASSIGNMENT 10

Srinitha Beerelly

8 JAN , 2021

## 1 Problem Statement :

Consider the given circuit

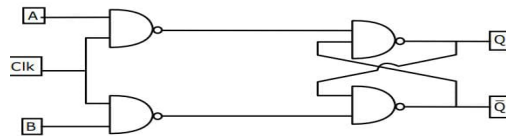

in this circuit, the race around

- (A) does not occur
- (B) occurs when CLK=0
- (C) occurs when CLK=1 and A=B=1
- (D) occurs when CLK=1 and A=B=0

## 2 Explanation:

$$Q_{next} = \overline{\overline{A} \cdot \overline{CLK} \cdot \overline{Q}}$$
$$= A \cdot CLK + Q$$

$$\overline{Q}_{next} = B \cdot CLK + \overline{Q}$$

If CLK = 1 and A = B = 1

then  $Q_{next} = 1$

$$\overline{Q}_{next} = 1$$

then no race around

If CLK = 1 and A = B = 0

then  $Q_{next} = Q$

$$\overline{Q}_{next} = \overline{Q}$$

then no race around

Thus race around does not occur in the circuit

### 3 Answer

the answer to the given question is (A)

To Be Noted : Race around is applicable only for J-K flip flop when  $CLK = 1$  and  $A=B=1$ . But the given circuit is S-R flip flop so no race around occurs.

### 4 STATE TRANSITION TABLE

TABLE 1			
Present state(Q)	input(S)	input(R)	Next state( $Q_n$ )
0	0	0	0
0	0	1	0
0	1	0	1
0	1	1	X
1	0	0	1
1	0	1	0
1	1	0	1
1	1	1	X